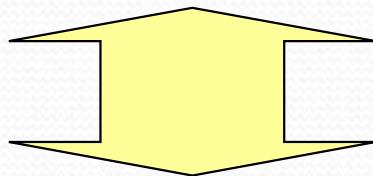


Norton's theorem



نظرية نورتن

B –Rationale

مبررات الوحدة

- It is very important to study Norton's theorem.
- Also to study how apply the three step to the save theorem .

الفكرة المركزية Central Idea

- Definition Norton's theorem .
- How we find the current at each resistance in the net work by the above theorem .

D- Aim of lecture

To let the student be able to identify the analyses net work by using Norton's theorem.

Pretest

الاختبار القبلي


Define : short circuit , Open circuit

solution


Short circuit : هي دائرة القصر التي يمر فيها جميع التيارات لنفس الدائرة الكهربائية لعدم وجود مقاومة فيها أي أن قيمة مقاومتها تكون صفراء .

Open circuit : هي الدائرة المفتوحة التي تكون مقاومتها ملا نهائية وقيمة التيار المار فيها يكون صفراء .

Ex. :- Find (I_L) for the cct shown

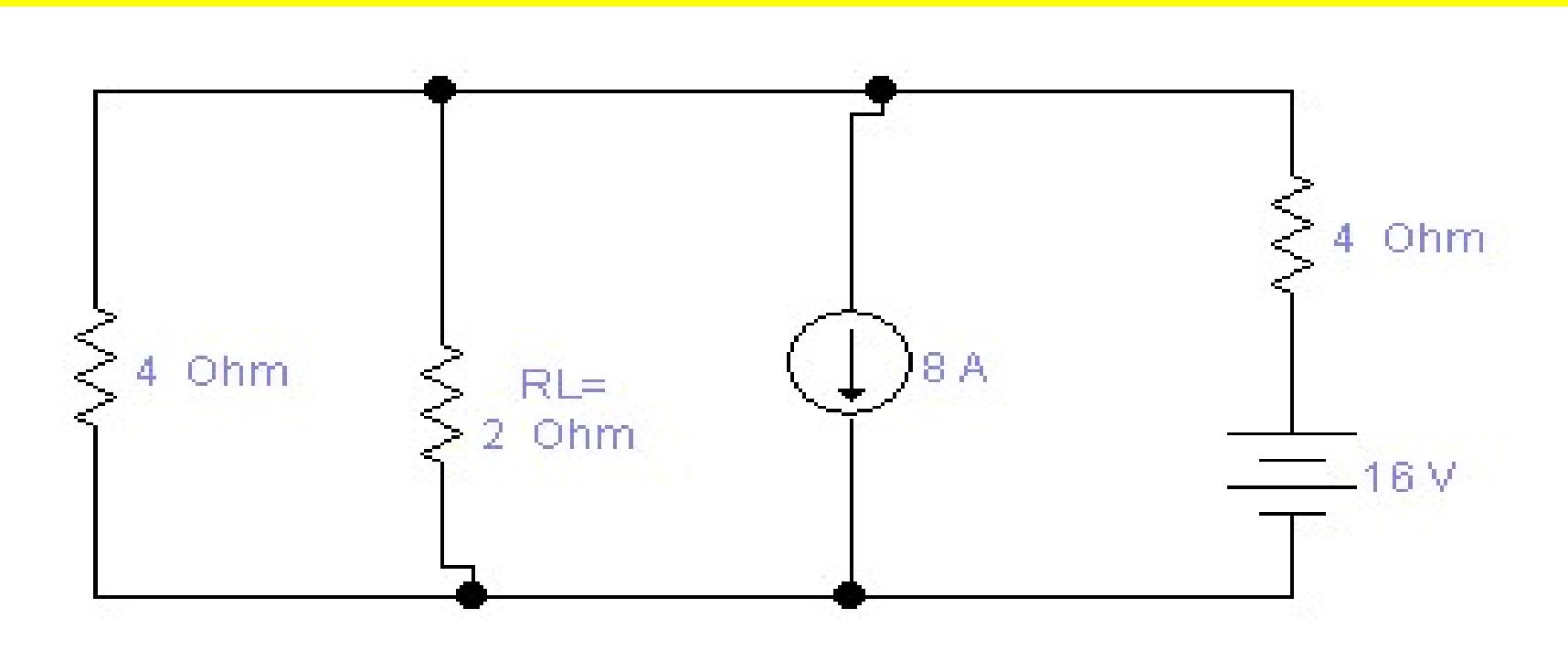

Solution; 1- To find $I_{s.c}$

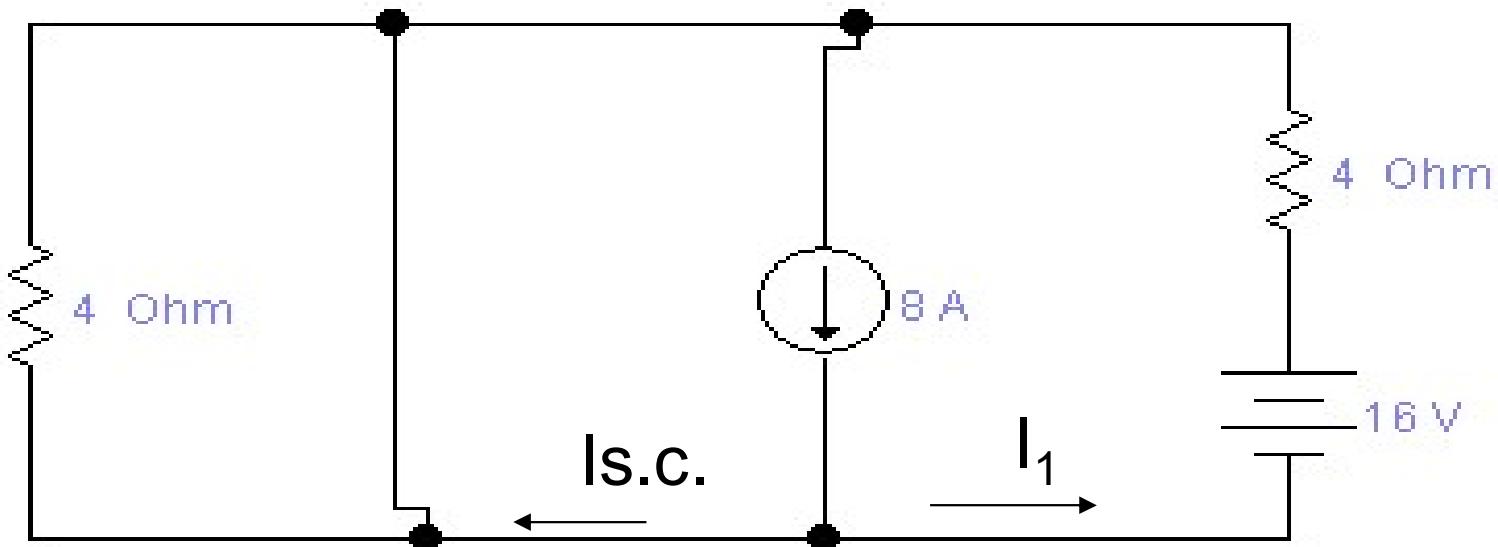


$$I_1 = 16/4 = 4 \text{ A}$$

$$8 - I_1 - I_{s.c.} = 0 \quad (\text{K.c.L})$$


then; $I_{s.c.} = 4 \text{ A} = I_N$

2- TO find R_N :

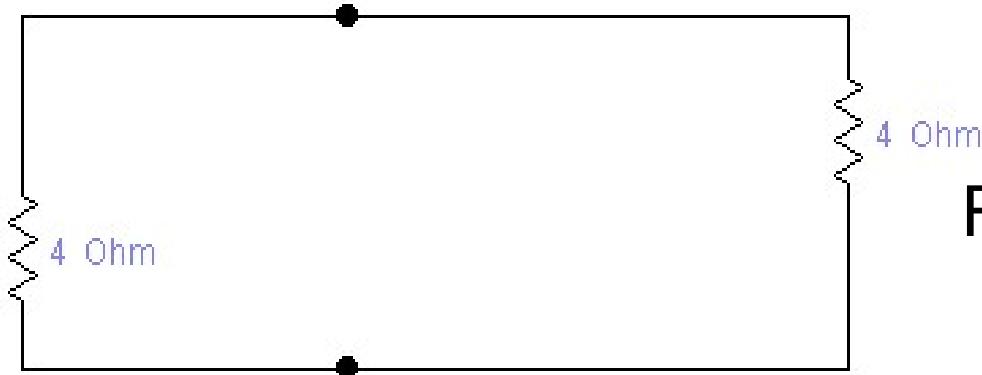


$$R_N = (4 \times 4) / 8 = 2\Omega$$

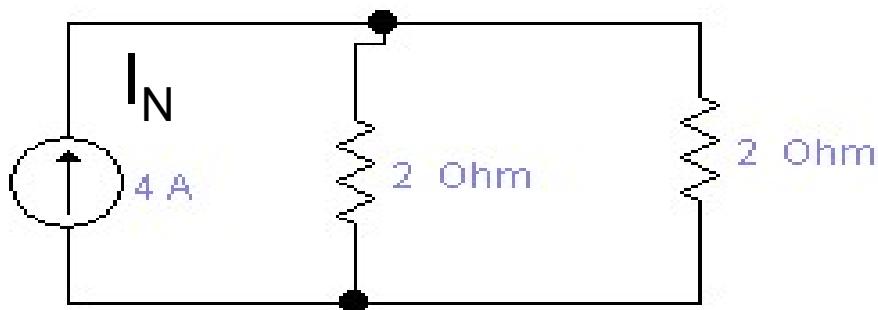3- Drawing Norton's equivalent and calculate I_N




$$I_N = (4 \times 2) / (2 + 2) = 2A$$

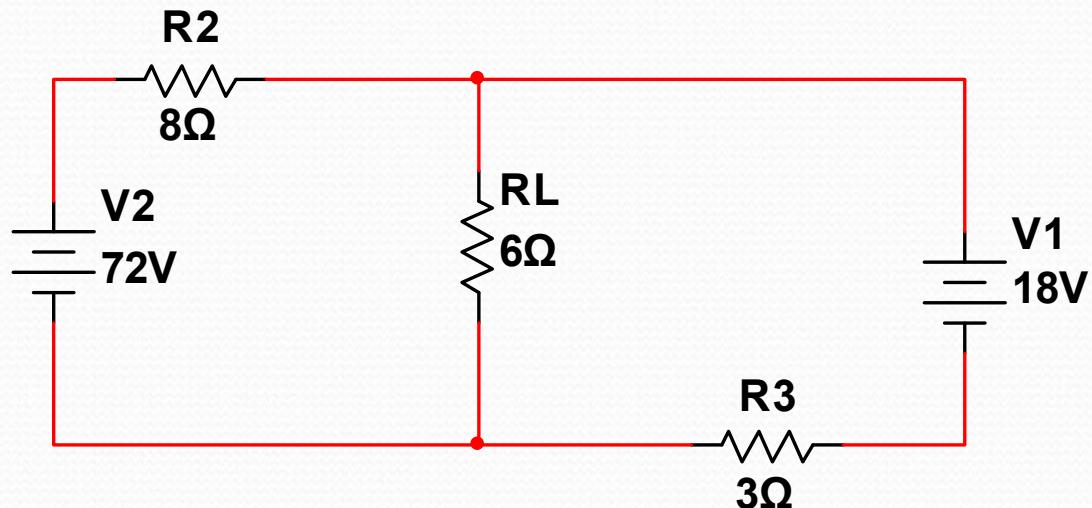Home work: For the cct. Shown find
 $(I_{Lat6\Omega})$ using Norton's theorem



Solution


1

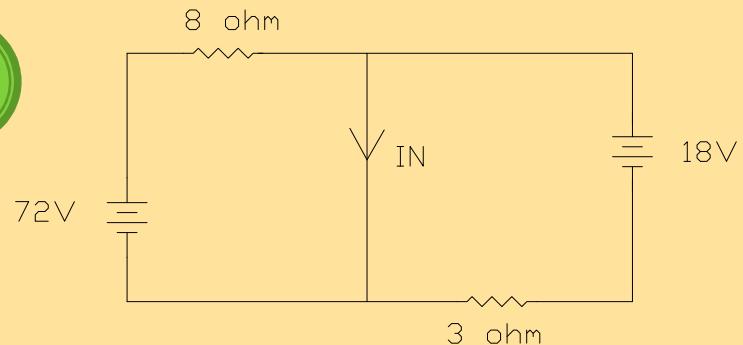

$$I_{sh} = I_1 + I_2 \quad , \quad I_1 = 72/8 = 9A$$


$$I_2 = 18/3 = 6A \therefore I_{sh} = 15A$$

2

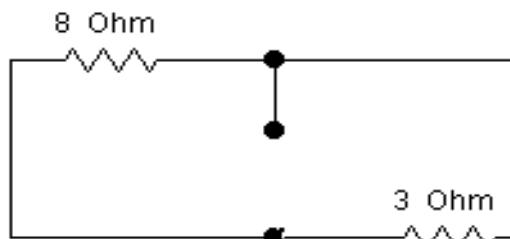

$$RN = 3 \times 8 / 11 = 24 / 11 = 2.18\Omega$$

3

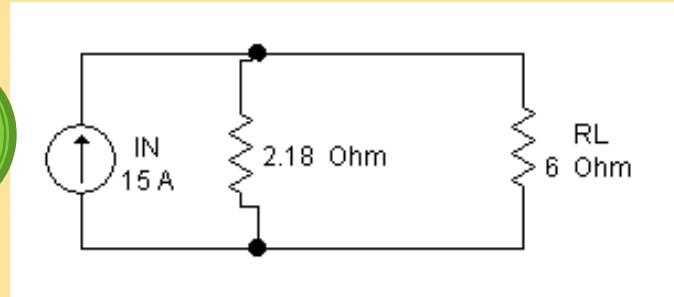

$$IL = (15 \times 2.18) / (2.18 + 6) = 4A$$