



Suppers position theorem



نظرية التركيب أو التطابق

Aim of lecture : To let the student be able to identify the analyses net worke by using Suppers position theorem

B –Rationale

مبررات الوحدة

- It is very important to study Suppers position theorem

C – Central الفكرة المركزية

Idea

- Definition Suppers position theorem
- To calculate the lowed current flows from each source and to find the result from the total currents.

Pretest الاختبار القبلي

Define : Current load (IL) ,draw Norton equivalent

Solution

(تيار الحمل)


هو التيار المار خلال مقاومة الحمل المراد حساب تيارها

IL:




$$I_L = I_n \times R_N / (R_N + R_L)$$

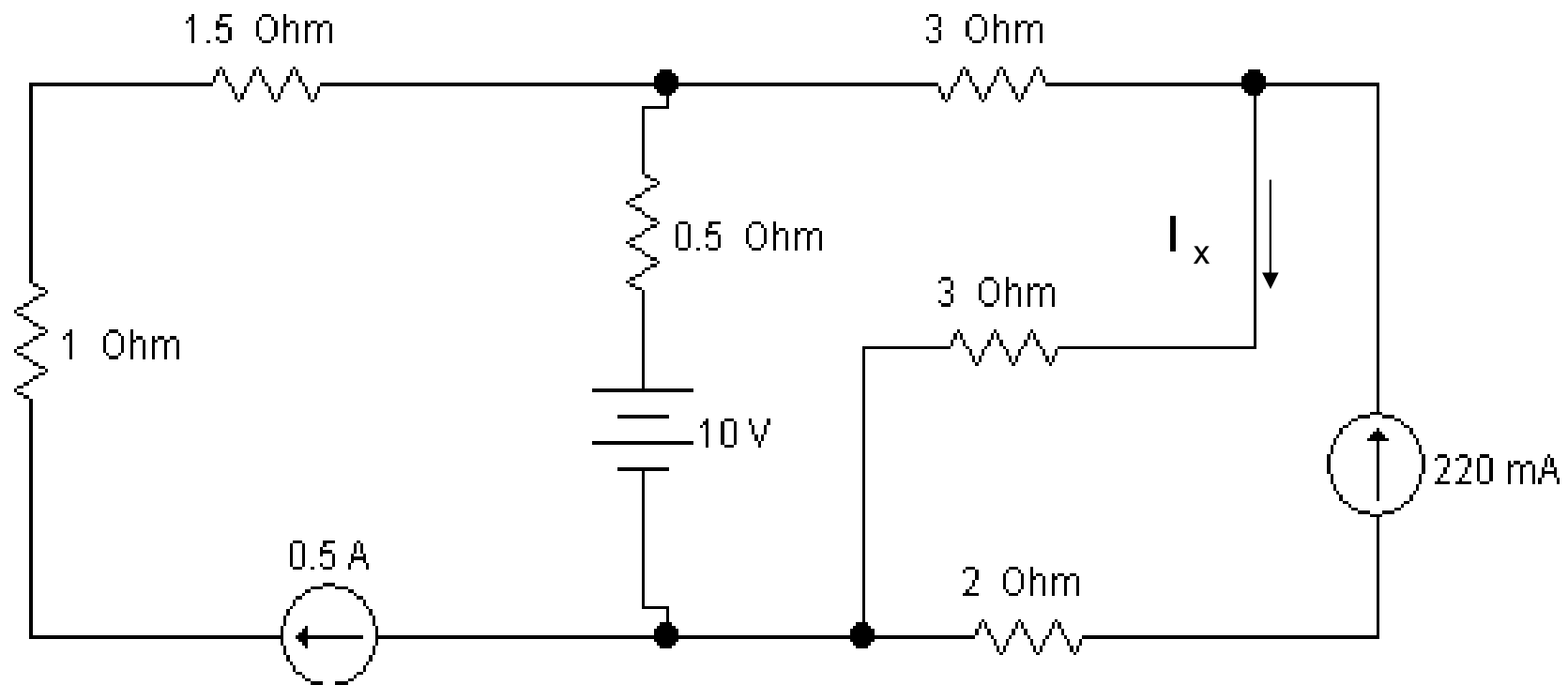Ex. For the cct. Shown using
supper position theorem to find (I_x
)




Solution:- 1- Effect of 0.5A only

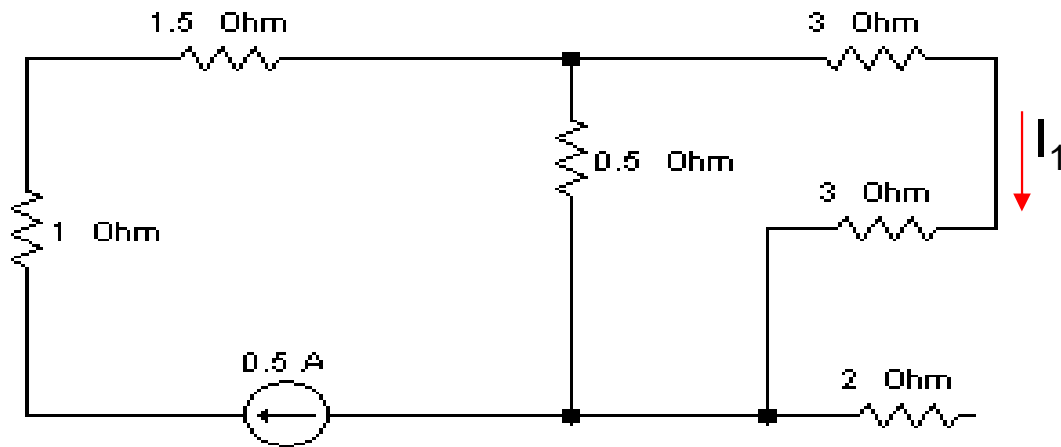


$$I_1 = 0.5 \times (0.5) / (0.5 + (3+3)) = 0.038 \text{ A} \downarrow$$

2- Effect of 220mA only

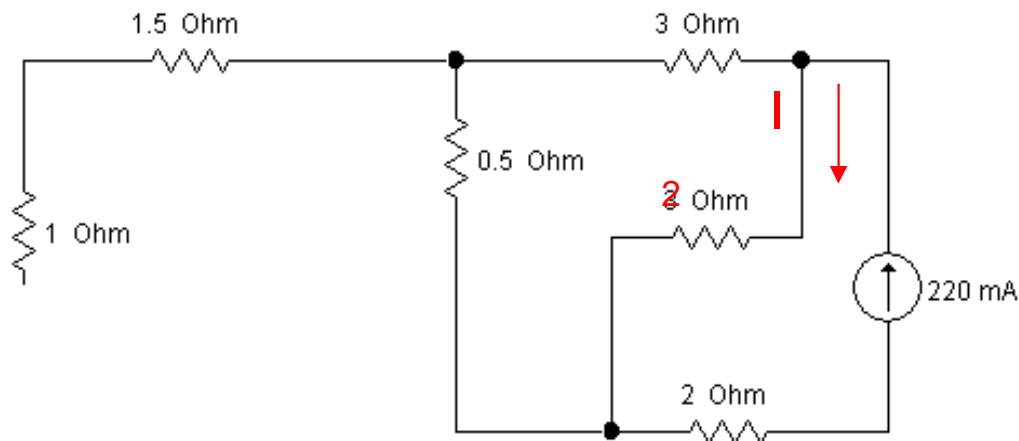

$$I_2 = 0.22 \times (3 + 0.5) / (3.5 + 3) = 0.118 \text{ A} \downarrow$$


3- Effect of 10v only

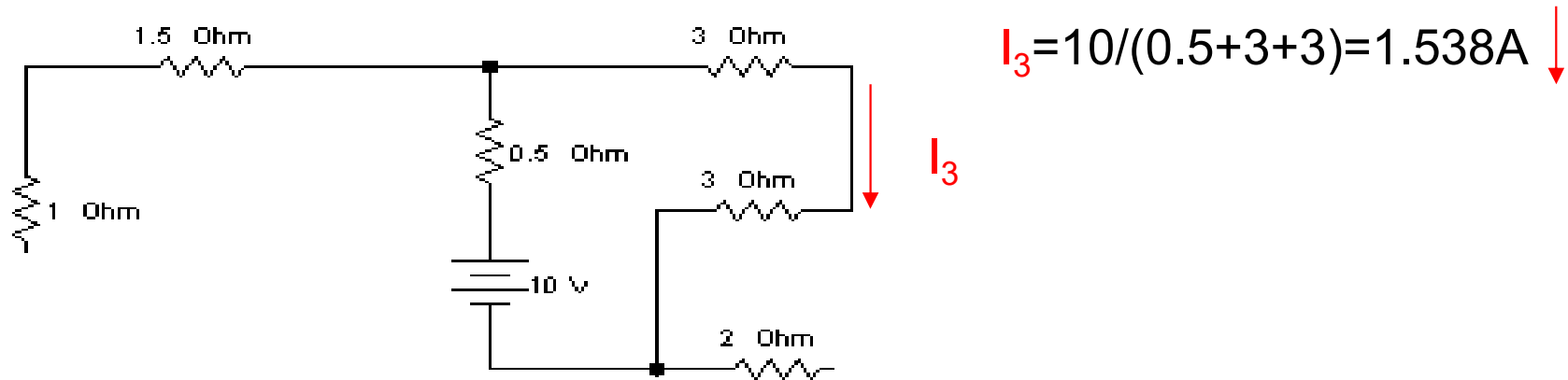

$$I_3 = 10 / (0.5 + 3 + 3) = 1.538A$$

$$\text{Then } I_x = I_1 + I_2 + I_3 = 1.694A$$

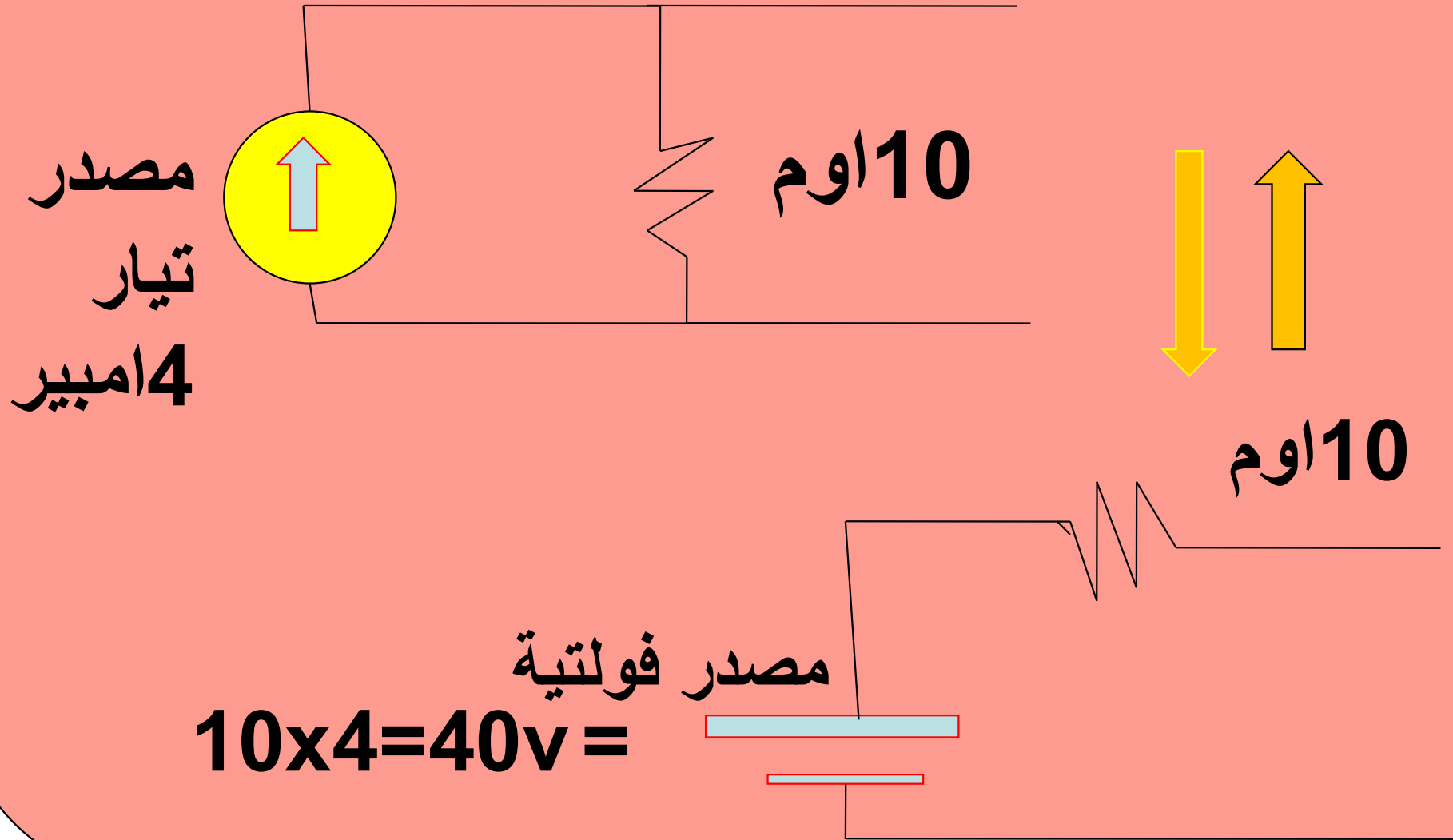كيفية تحويل مصدر التيار إلى مصدر فولتية وبالعكس



Note

Maximum power transfer

• انتقال أظم قدرة

When $R_L = R_{in}$ there is P_{maximum} transfer to the load

$$R_L = R_{in}$$


$$I_L = V / (R_{in} + R_L) = V / 2R_{in} \quad \text{But } P = I^2 \cdot R$$


$$P_{\text{max.}} = I_L^2 \cdot R_L$$

$$P = (V / 2R_L)^2 \times R_L = V^2 \times 4R_L$$

Then ; at Thevinins equivalent

$$P_{\text{max}} = V_o.c^2 / 4R_{th}$$

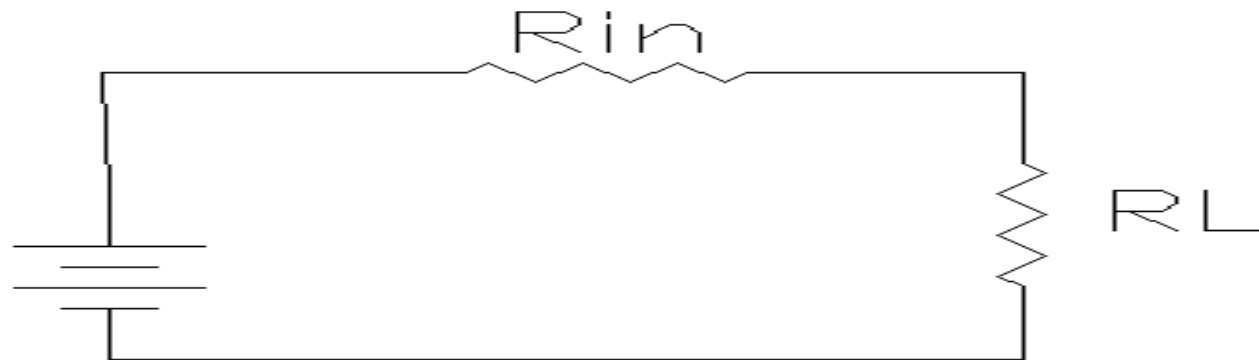


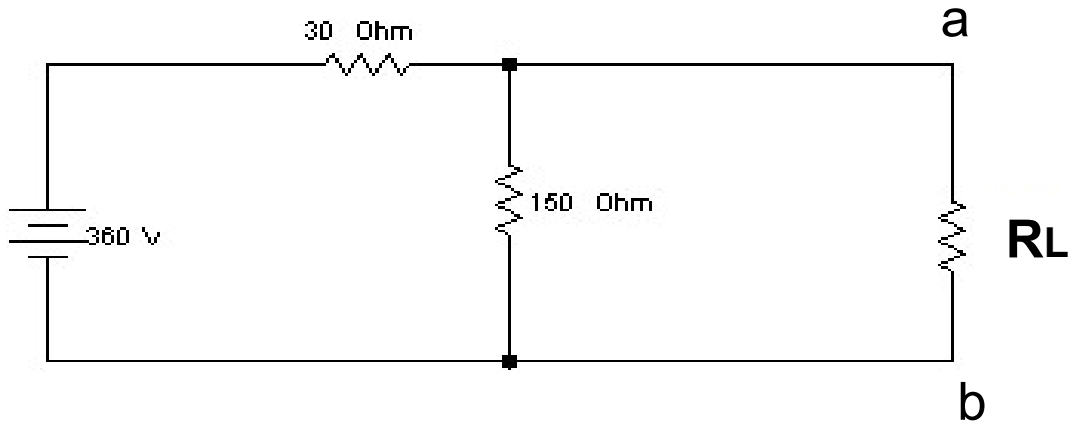


Ex. : Find R_L
for max. p . T
and calculate P_{max} .

Solution

$R_L = R_{th}$ then

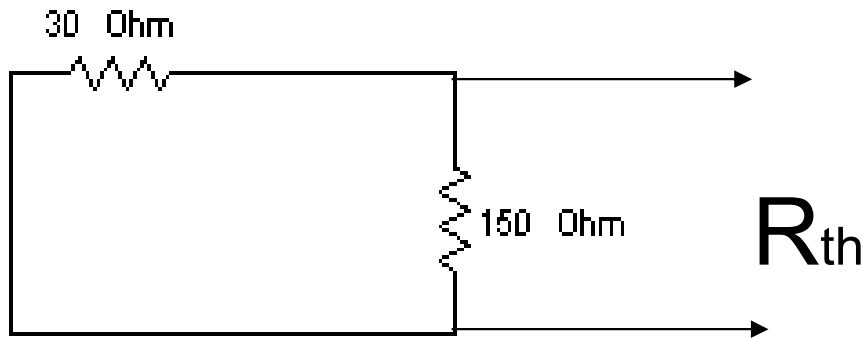
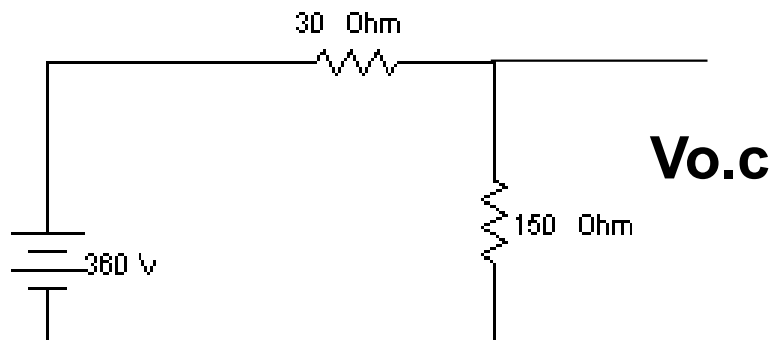
$$R_{th} = (30 \times 150) / (30 + 150) = 25 \text{ ohm} = R_L$$



$$V_{o.c} = 150 \times 360 / (30 + 150) = 300 \text{ v}$$


$$P_{max} = V_{o.c}^2 / 4 R_{th} =$$

$$(300)^2 / (4 \times 25) = 900 \text{ watt}$$


Posttest

الاختبار الـبعدي

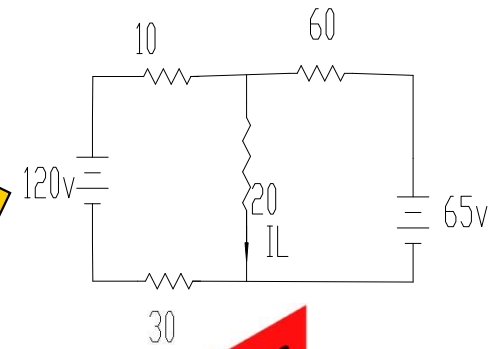For the cct. Shown find I_L by using super position theorem



Solution

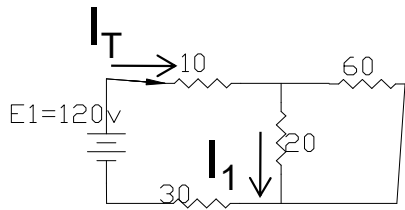


(1)

$$E_1 = 120\text{V}, E_2 = 0, R_T = (60 // 20) + 10 + 30 = (20 \times 60) / 80 + 40 = 55\Omega$$

$$I_T = 120 / 55 = 2.182\text{A},$$
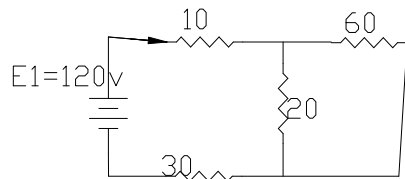
$$\therefore I_1 = 60 / (60 + 20) \times 2.182 = 1.64\text{A}$$



(2)

$$E_1 = 0, E_2 = 65\text{V}, R_T = [(10 + 30) // 20] + 60 = (40 \times 20) / 60 + 60 = 73\Omega$$

$$I_T = 65 / 73 = 0.89\text{A}, \therefore I_2 = 40 / (40 + 20) \times 0.89 = 0.59\text{A}$$

$$\therefore I_L = I_1 + I_2 = 1.64 + 0.59 = 2.23\text{A} \downarrow$$

